

## ASSIGNMENT - 4


### 3-bit Gray Code Counter

#### Approach:

We have used 8 states to implement the 3-bit Gray code counter. The states are as follows :  $S_0 = 000$ ,  $S_1 = 001$ ,  $S_2 = 010$ ,  $S_3 = 011$ ,  $S_4 = 100$ ,  $S_5 = 101$ ,  $S_6 = 110$ ,  $S_7 = 111$ .

There is an input pulse of 1 bit having value = 1. With each input pulse, a state transition takes place. Output is high only when the state changes from  $S_7$  to  $S_0$ . Otherwise, the output is zero.

#### State transition diagram :

 

### Excitation tables :

We are using T-flip flops for implementing the gray code counter. The excitation table for the T-flip flop can be shown as follows :

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

EXCITATION TABLE  
FOR T-FLIP FLOP.

We represent the MSB of the states as  $Q_c$  and the LSB as  $Q_a$ . The superscript 't' denotes the present state and the superscript 't+1' denotes the next state. The excitation table for all the 3 bits is as follows :

$Q_c^t$	$Q_b^t$	$Q_a^t$	$Q_c^{t+1}$	$Q_b^{t+1}$	$Q_a^{t+1}$	$T_c$	$T_b$	$T_a$	out
0	0	0	0	0	1	0	0	1	0
0	0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	0	0	0	0
0	1	0	1	1	0	1	0	1	0
1	1	0	1	1	1	0	0	1	0
1	1	1	1	0	1	0	1	1	0
1	0	1	1	0	0	0	0	1	0
1	0	0	0	0	0	1	0	0	1

EXCITATION TABLE

### State Table:

(NS, output)	
Present State	input 1'b1
$S_0$	$(S_1, 0)$
$S_1$	$(S_2, 0)$
$S_2$	$(S_3, 0)$
$S_3$	$(S_4, 0)$
$S_4$	$(S_5, 0)$
$S_5$	$(S_6, 0)$
$S_6$	$(S_7, 0)$
$S_7$	$(S_0, 1)$


STATE TABLE

### Transition and Output Table:


Present state	Next state	Output
$S_0$	$S_1$	0
$S_1$	$S_2$	0
$S_2$	$S_3$	0
$S_3$	$S_4$	0
$S_4$	$S_5$	0
$S_5$	$S_6$	0
$S_6$	$S_7$	0
$S_7$	$S_0$	1

TRANSITION AND  
OUTPUT TABLE

**K-maps:**

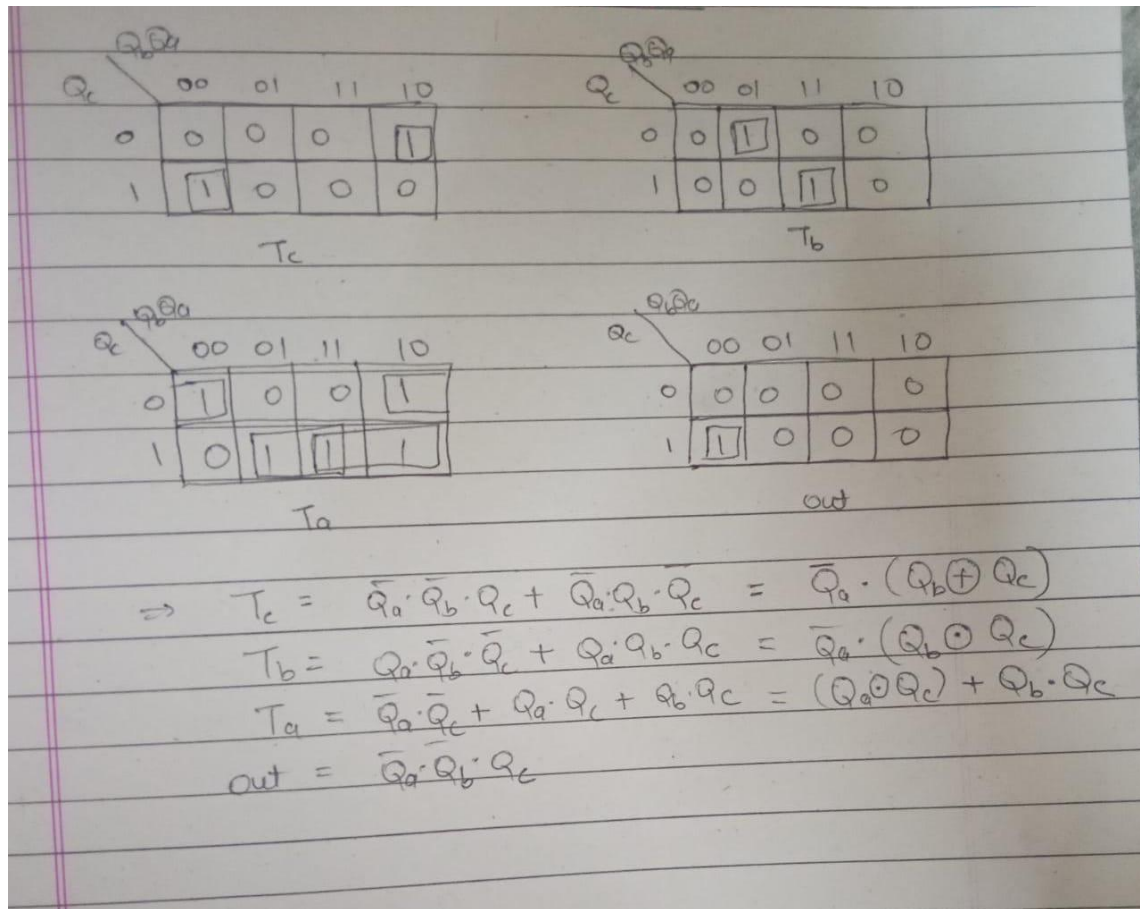

**Circuit Diagram :**

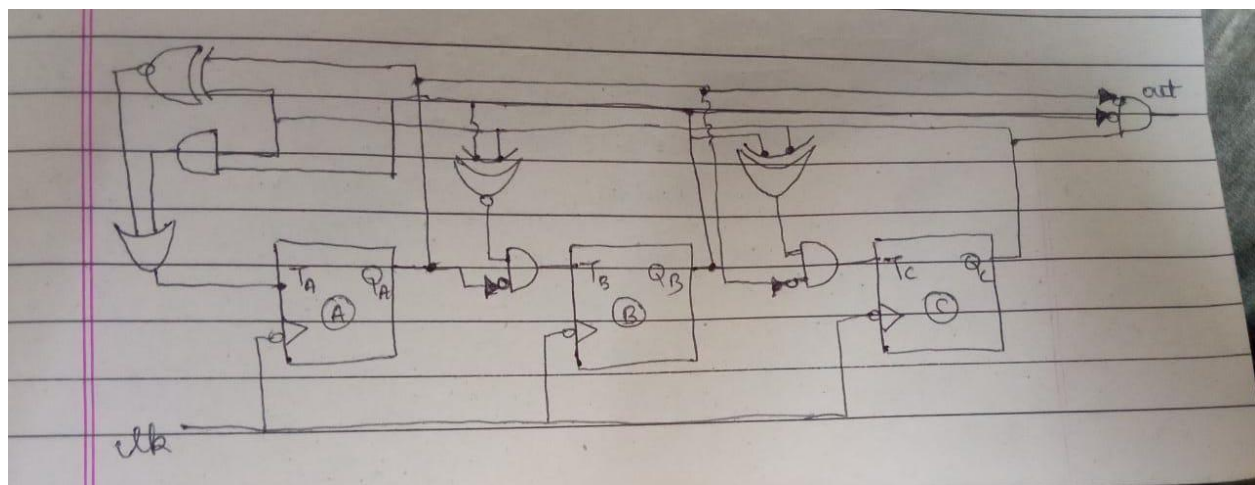




## 8-bit Adder/Subtractor

We are given two 8-bit numbers (namely A and B) and we have to either add or subtract them.  
opcode = 0 for addition and  
opcode = 1 for subtraction.

### Circuit:

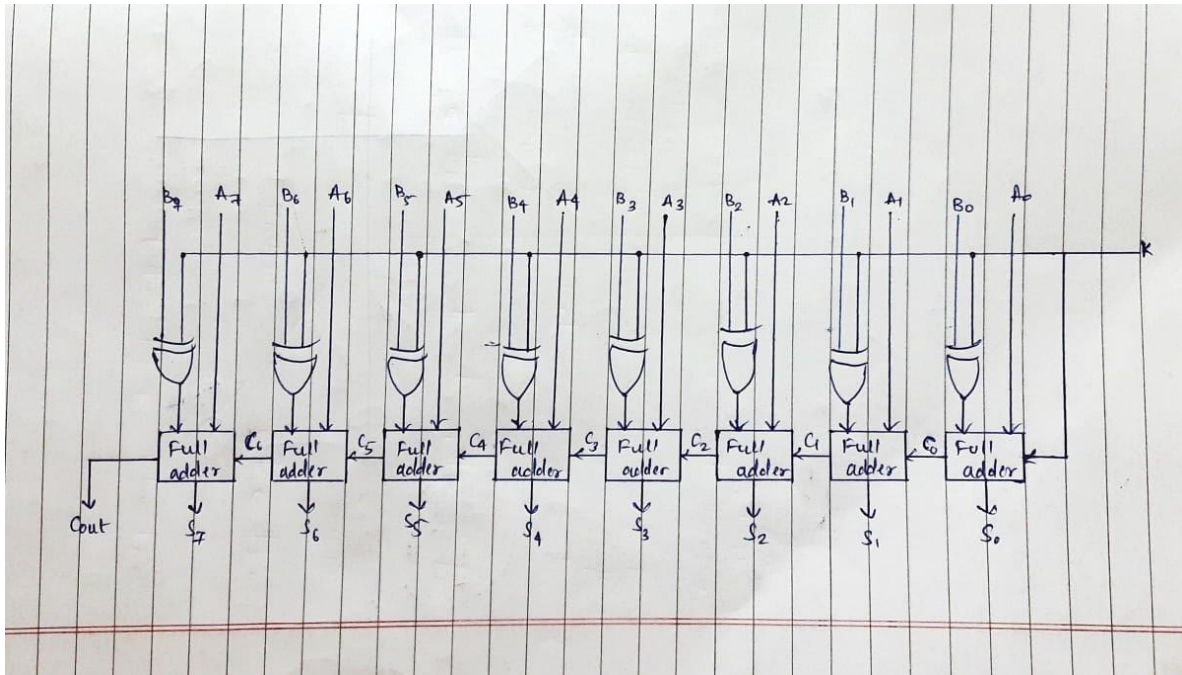

Here,  $A_7, A_6, \dots, A_0$  are the input bits of A and  $B_7, B_6, \dots, B_0$  are the input bits of B.  
 $S_7, S_6, \dots, S_0$  are the output bits of the result.  
 $C_{out}$  is the carry out and k is the opcode.

### Approach:

We have implemented an 8-bit adder/subtractor using Full Adder and XOR gate.

For addition,  $k=0$  and

For subtraction,  $k=1$

Truth table for XOR gate is as follows:

X	Y	XOR
0	0	0
1	0	1
0	1	1
1	1	0

We observe,

When  $Y=0$ , the output XOR for a given input  $X$  is  $X$  itself and

When  $Y=1$ , the output XOR for a given input  $X$  is  $\bar{X}$ .

So, when we want to add the number we simply pass  $k=0$  and

when we want to subtract the number (that is adding 2's complement) we pass  $k=1$ .

For adding  $A$  and  $B$ , the XOR of  $B$  and  $k=0$  simply gives  $B$ , and we do the bitwise addition of  $A$  and  $B$  using 1-bit Full Adder by feeding the carry out of the previous bit to the next bit.

We do the subtraction by 2's complement method. The XOR of  $B$  and  $k=1$ , gives  $\bar{B}$  and for LSB of result we add  $k=1$ , as 2's complement is obtained by adding one to the 1's complement of  $B$ . Hence, the result is obtained by adding 2's complement of  $B$  to  $A$  using 1-bit Full Adder by feeding the carry out of the previous bit to the next bit.

Full Adder Truth Table:

$X$	$Y$	$C_{in}$	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

We observe,

$$\text{Sum} = X \oplus Y \oplus Z$$

$$\text{Carry} = X \cdot Y + X \cdot C_{in} + C_{in} \cdot Y$$

**Overflow condition:**

Overflow occurs when  $C_6 \neq C_{out}$ .

No overflow when  $C_6 = C_{out}$ .

Truth Table:

$C_6$	$C_{out}$	Overflow
0	0	0
0	1	1
1	0	1
1	1	0

Therefore,

$$\text{Overflow} = C_6 \oplus C_{out}.$$